

Implementation of T Flip-Flop using D Flip -Flop

Susi

August 25, 2022

1 Abstract

This manual shows Design of T flip-flop using D flip-flop

2 Components

Component	Value	Quantity
Bread board	-	1
Arduino	Uno	1
LED	-	2
IC	7474	1
Jumper Wires	-	20

Table 1:

3 Procedure

- 1.Connect 5V of the Arduino to the Top Green of the Bread Board and GND to the Bottom Green.
- 2.Connect D13 pin in the Arduino to the 3 (CLK) pin of the IC 7474.
- 3.Connect 1,4,14 pins of the IC 7474 to the VCC and 7 pin to the GND.
- 4.Connect Arduino D2 pin to the 2(1D) of the IC 7474.
- 5.Connect Arduino D5 pin to the 5 (1Q) of the IC 7474 .

6. Connect one LED + to the 5 pin of IC 7474 and GND the other terminal.
7. Connect another LED + to the 6 (!Q) pin of the IC 7474 and GND the other terminal.
8. Change the D12 pin in the Arduino from VCC to GND and observe the outputs.

4 Code

Execute the following code using the below provided link

<https://github.com/Susi9121/FWC/Code.ino>

5 Conversion table

Input	Intermediate Inputs			Outputs	
T	Q _n	!Q _n	T=D xor Q _n	Q _n	!Q _n
0	0	1	0	0	1
0	1	0	1	1	0
1	0	1	1	1	0
1	1	0	0	0	1

Table 2:

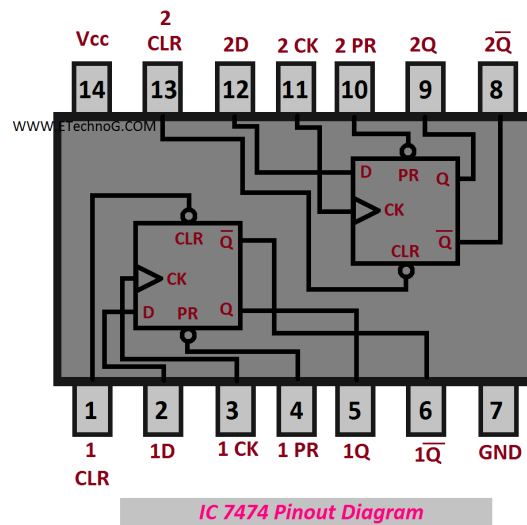


Figure 1: 7474

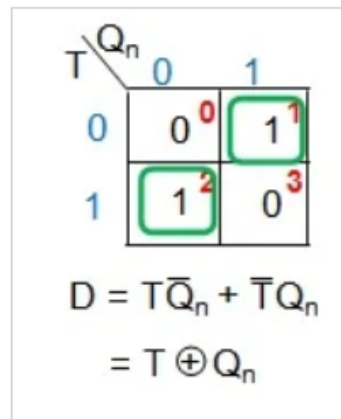


Figure 2: kmap

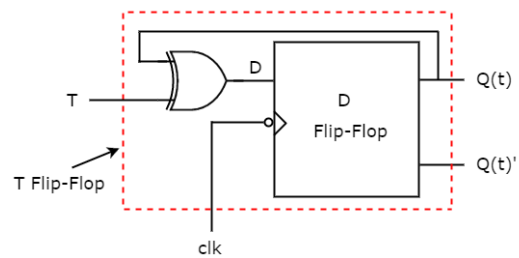


Figure 3: Circuit Diagram